

EEE-4384

Electronic Device and Circuits Lab

Experiment no: 02

Submitted By-

Name: Samin Abdullah

ID: 220041222

Section: 2 (B)

Programme: BSc in CSE

Department: CSE

Name of the Experiment: Study wave shapes of different types of clipping and clamping circuits

Objective:



- 1) To construct the clipping circuit and observe its corresponding wave shapes.
- 2) To construct the clamping circuit and observe its corresponding wave shapes.

Apparatus required: Diode, resistor, capacitor, Oscilloscope, standard project Board, Function / Signal generator, Connecting wires etc.

Task 1: To construct the clipping circuit and observe its corresponding wave shapes.



Series clipper circuit (with Diode and Resistor):

Positive Clipper:

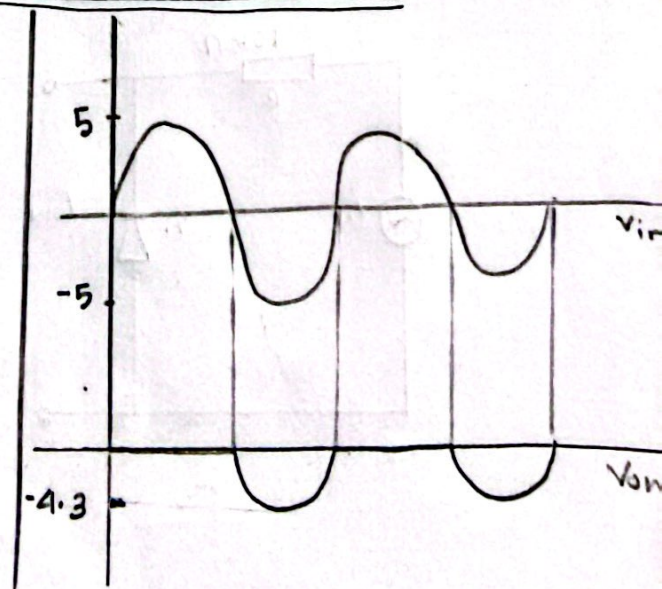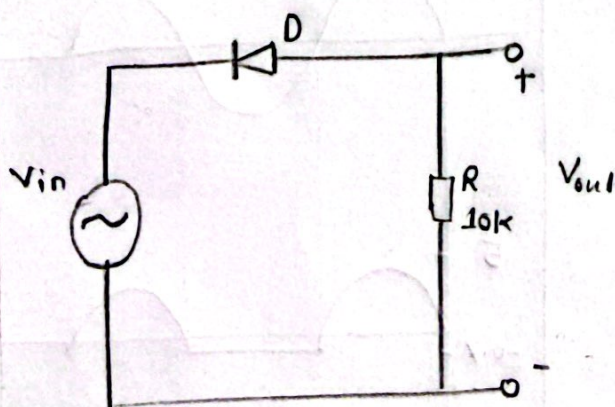





### Negative Clipper:

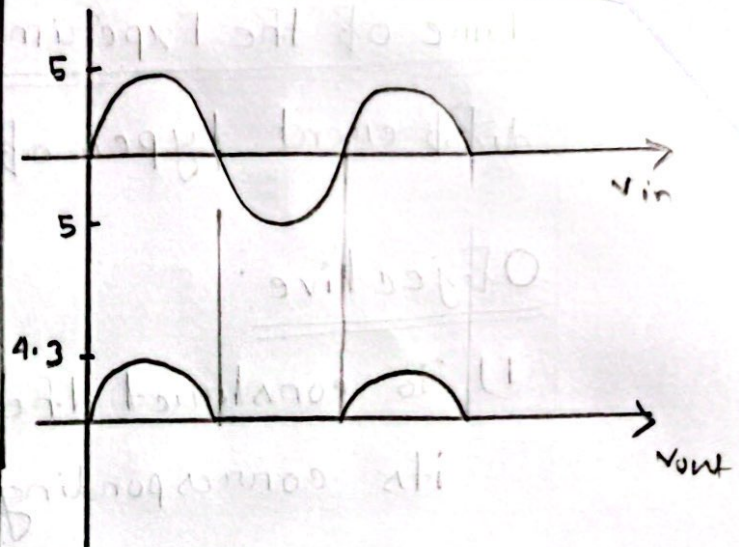
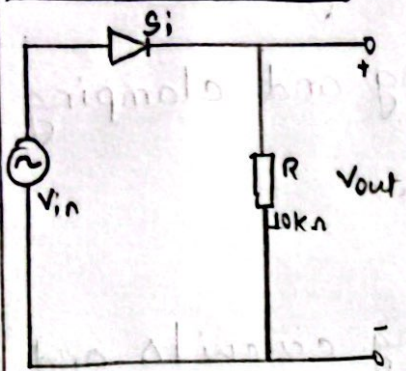


### Parallel Clipper Circuit (with Diode and Resistor):

#### Positive clipper:

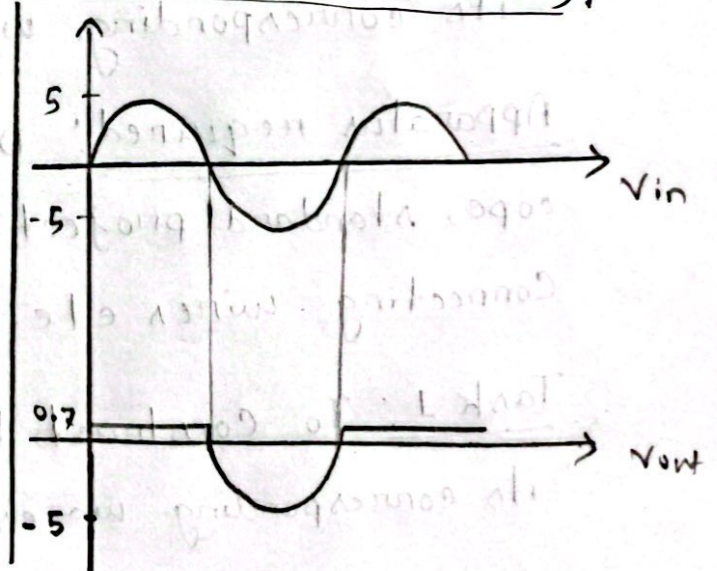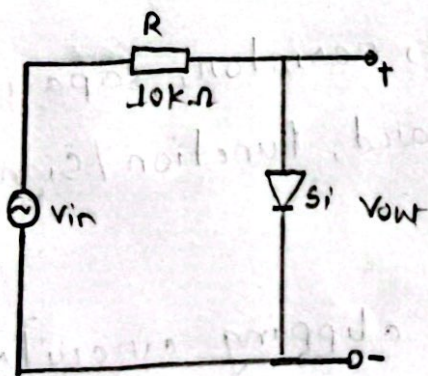



#### Negative clipper:

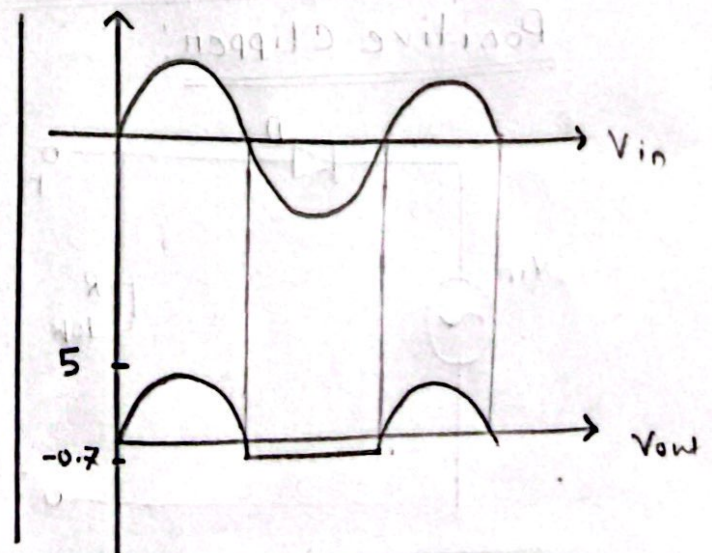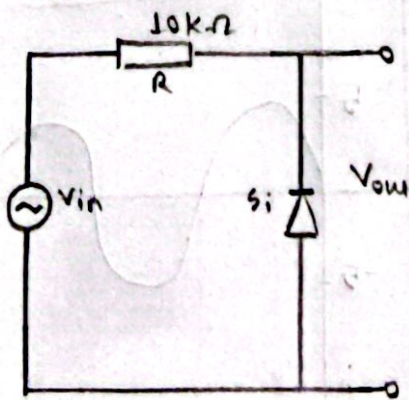





## Biased Series Clipper Circuit (with Diode and Resistor):



### Positive Clipper:

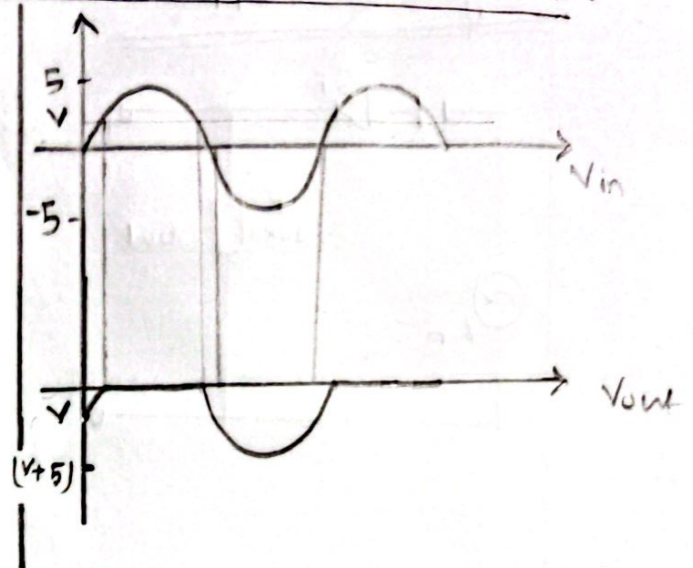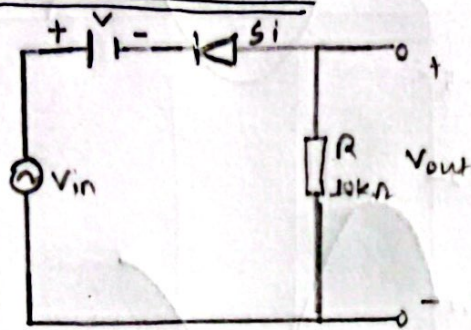

### Negative Clipper:

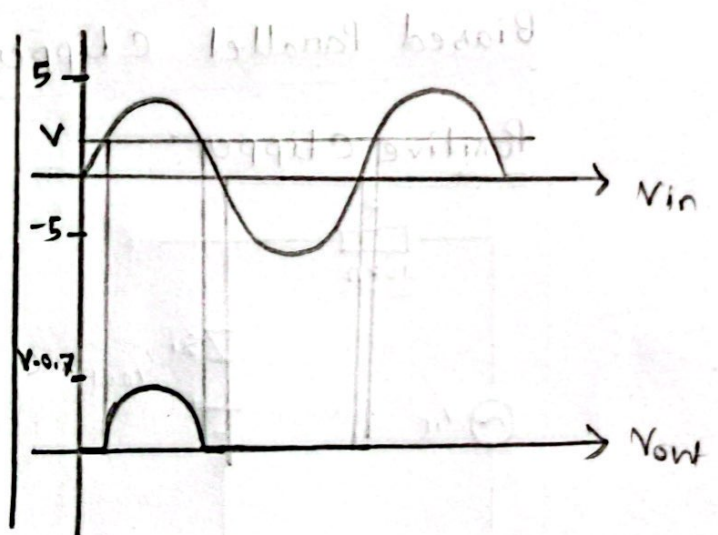
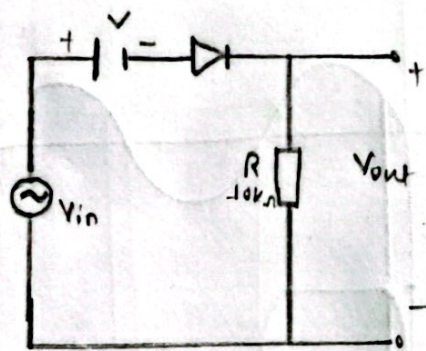


### Positive Clipper:

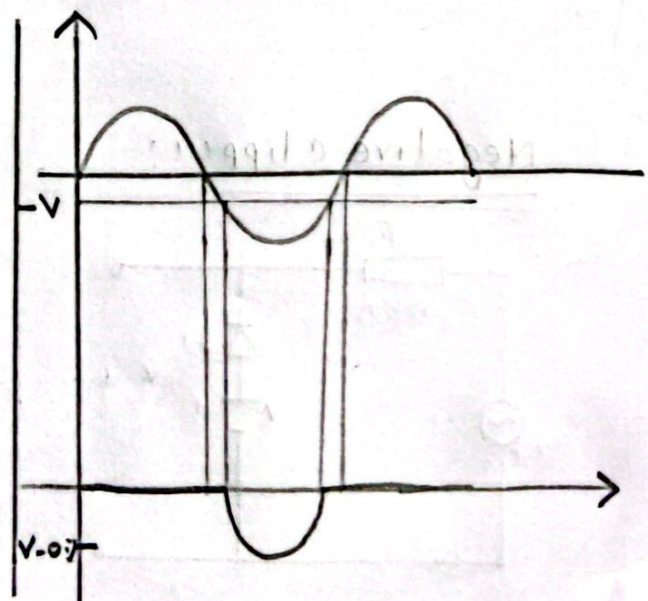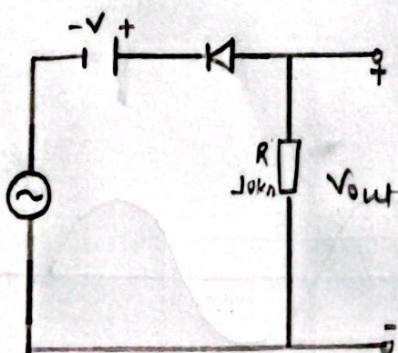





## Negative Clipper:

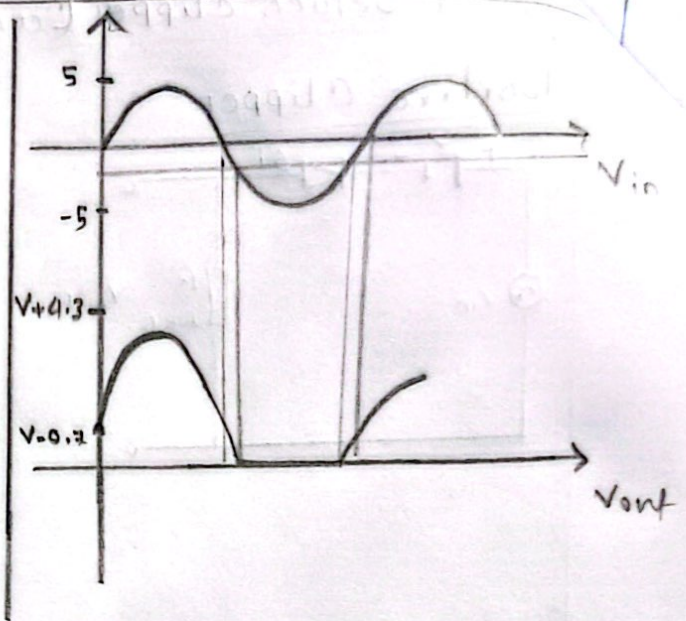
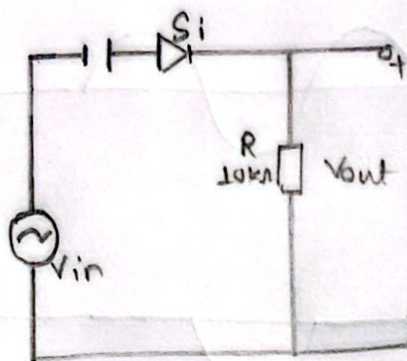


## Biased Parallel Clipper circuit (with diode and Resistor)

### Positive Clipper:

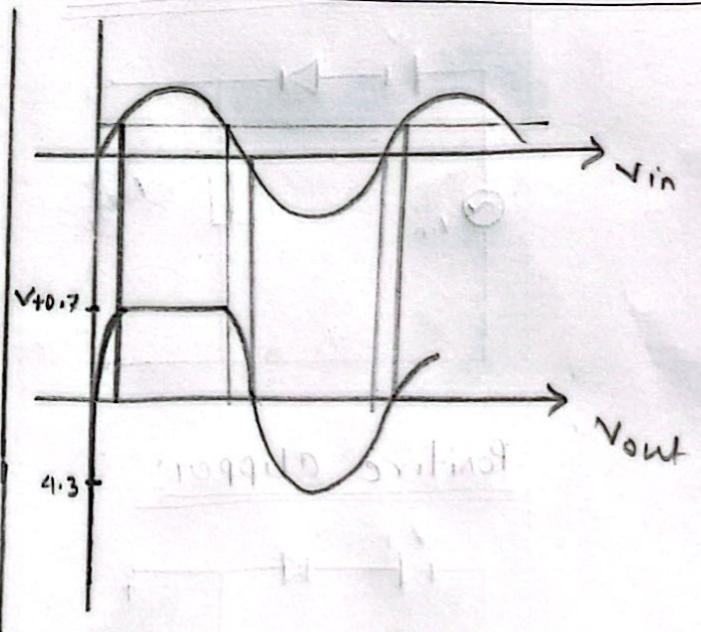
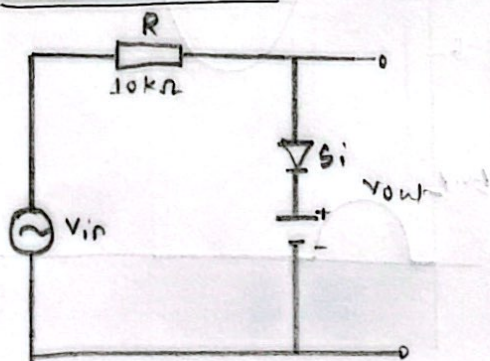


### Negative clipper:

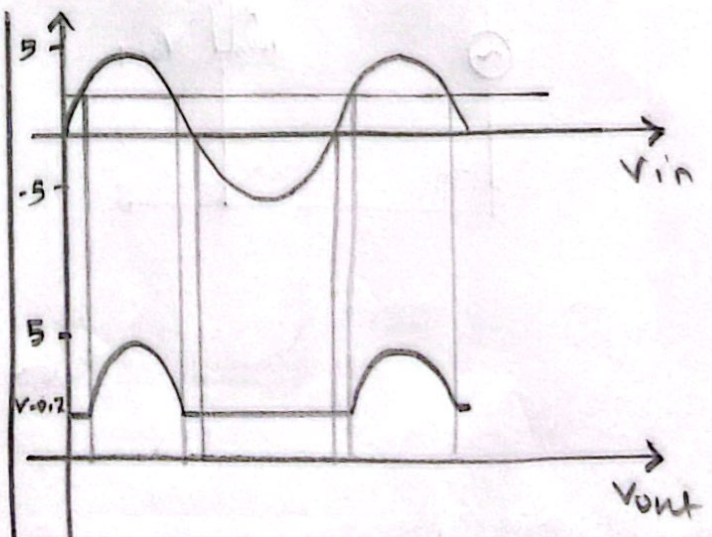
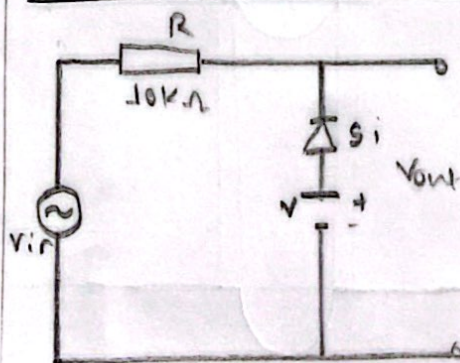






### Positive Clipper:

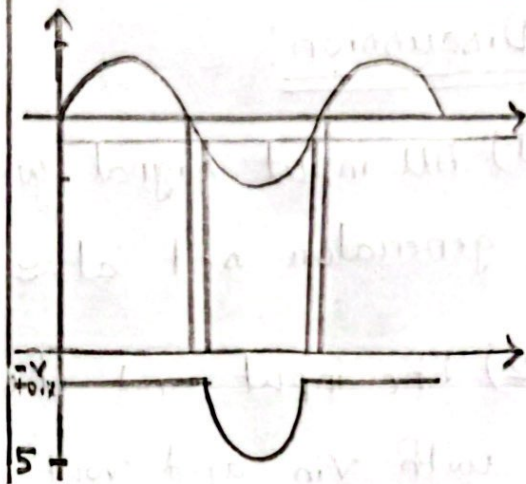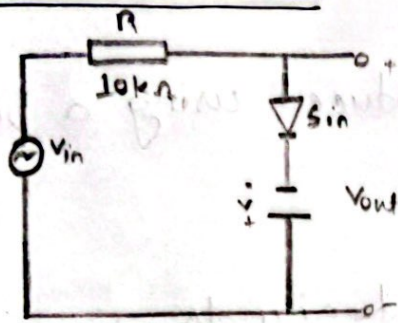

### Negative Clipper:

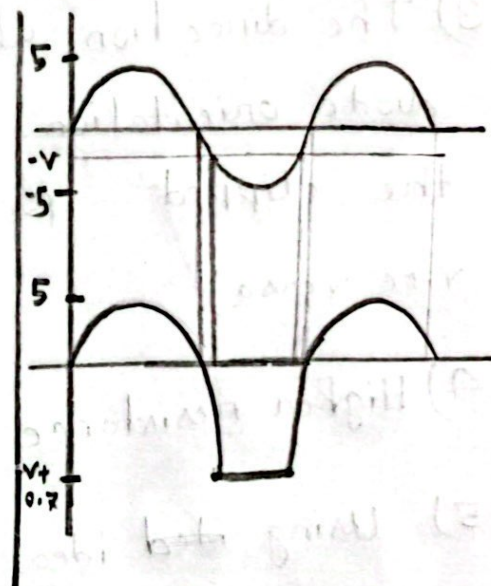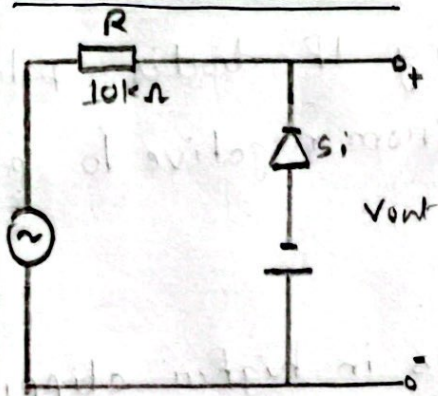
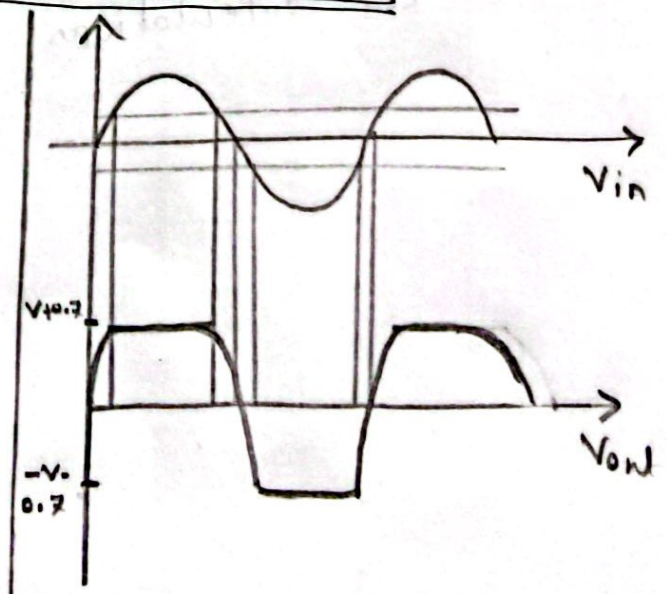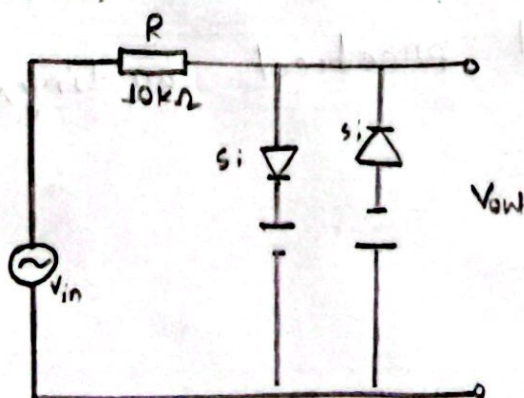
### Double Diode Biased Parallel Clipper Circuit:





### Discussion:

- 1) All input signals were produced using a frequency generator set at  $\approx 50\text{ Hz}$
- 2) The input and the output signals were labelled with  $v_{in}$  and  $v_{out}$  respectively.
- 3) The direction of the clipping is decided by the diode orientation. Reversing the diode's polarity swaps the clipped portion (from negative to positive or vice versa)
- 4) Higher resistance results in higher clipping.
- 5) Using ~~ideal~~ ideal diodes instead of practical ones would have lessened the difference between theoretical calculations and practical findings.





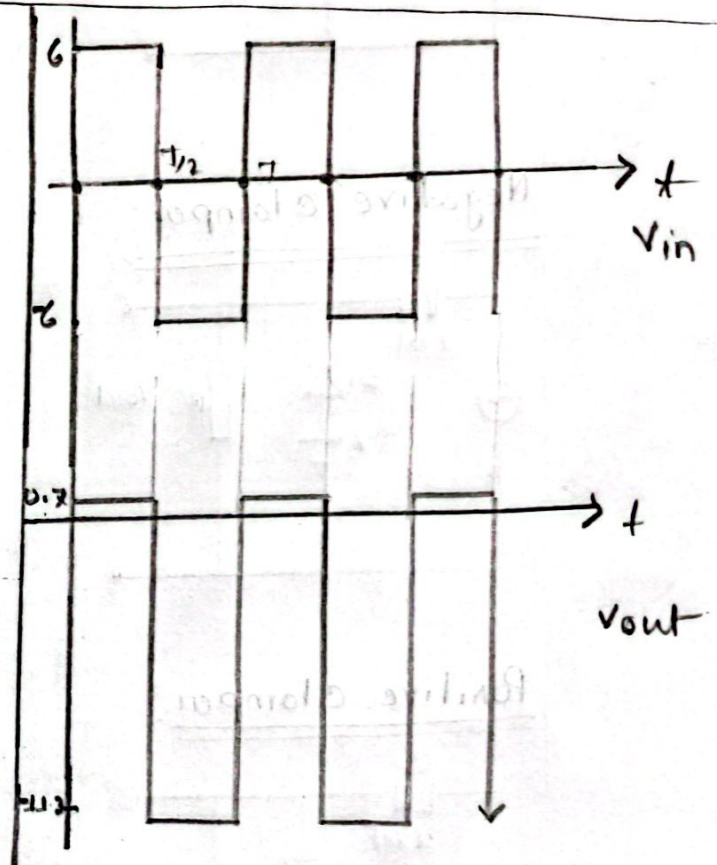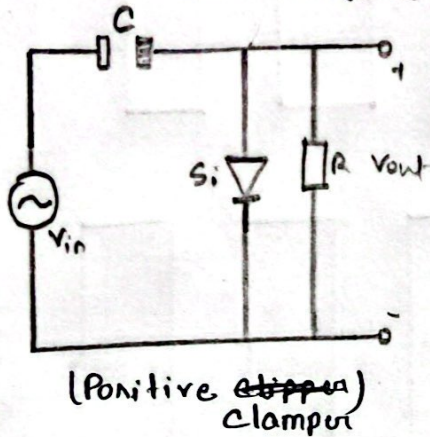Task 2: To construct a clamping circuit and observe its corresponding waveforms.

Series clamping circuit (with Capacitor, diode and Resistor):





Negative Clamper  
Clamper

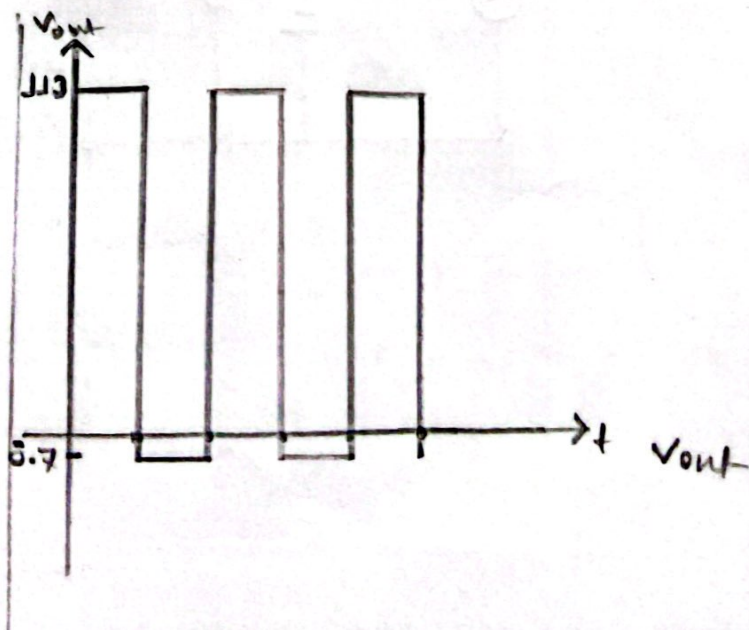
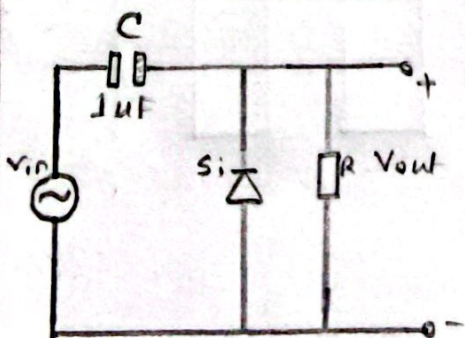






### Positive Clamper:

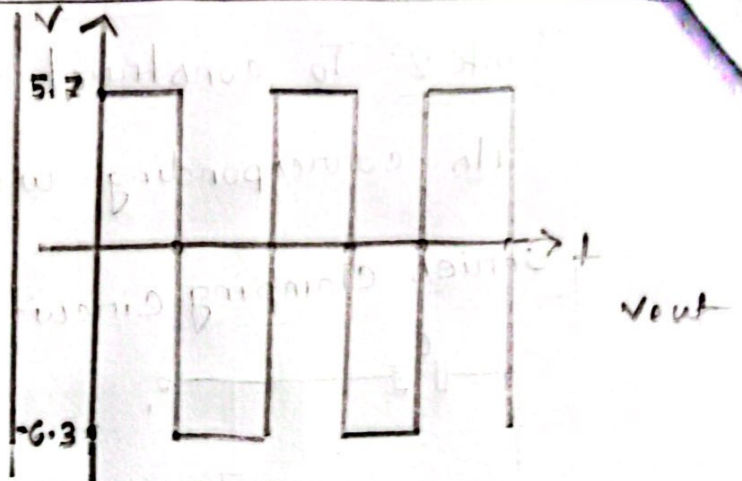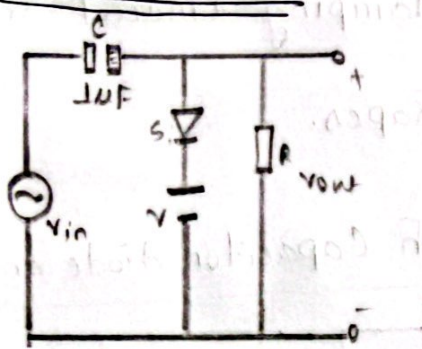

### Negative clamper:

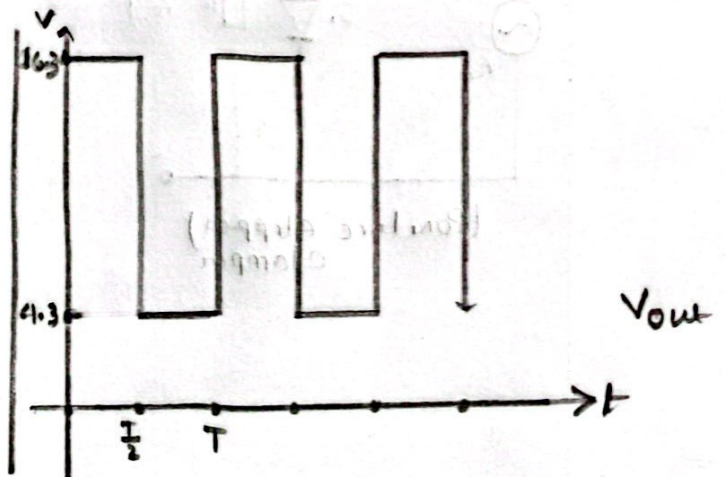
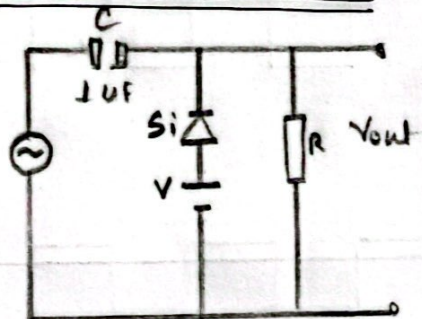


### Positive clamper:

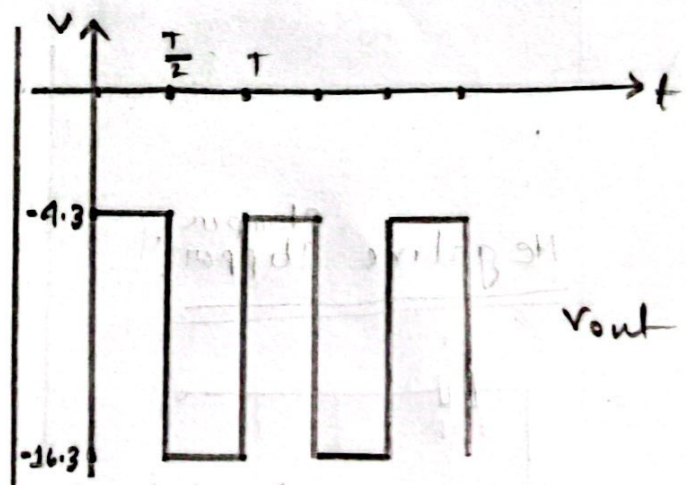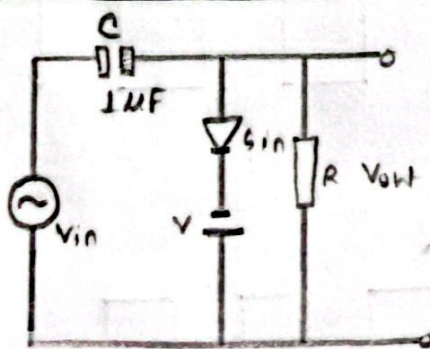



### Negative Clamper:

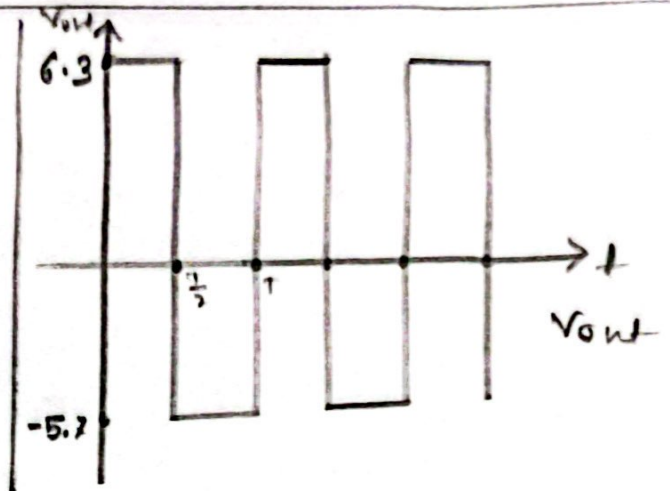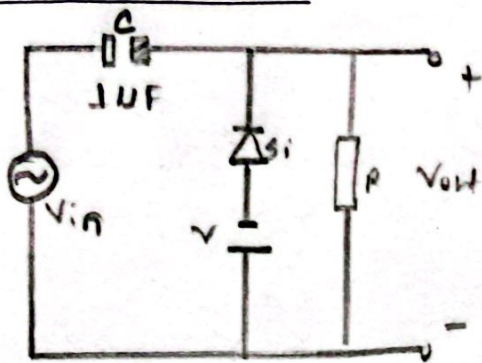

### Discussion:

- 1) Half of the time period ( $T/2$ ) must be less than the discharge time ( $T/2 < 5\tau$ , where  $\tau = RC$ )
- 2) Diode orientation affects the direction of DC level shifting. Reversing diode orientation changes the polarity of clamping.
- 3) clamper circuits ~~shift~~ shift the waveform up or down the  $x$ -axis.
- 4) Changing resistor and capacitor values in the circuit influence the clamping voltage and the time constant for discharging the capacitor.